

Clark Simper  
cws2522  
17510

Part 1

i. RCA\_4bits.v

```
`timescale 1ns / 1ps

module RCA_4bits
input clk,
input enable,
input [3:0] A,B,
input Cin,
output [4:0] Q
);

wire co0,co1,co2,co3;
wire [4:0] sum;

//Adding all 4 bits
full_adder s0(A[A(0)], B[B(0)], Cin(Cin), Ssum[0]), Cout(co0);
full_adder s1(A[A(1)], B[B(1)], Cin(co0), Ssum[1]), Cout(co1);
full_adder s2(A[A(2)], B[B(2)], Cin(co1), Ssum[2]), Cout(co2);
full_adder s3(A[A(3)], B[B(3)], Cin(co2), Ssum[3]), Cout(co3);
assign sum[4] = co3;

register_logic r0(clk,enable(enable),Data(sum),Q[Q]);

endmodule
```

full\_adder.v

```
`timescale 1ns / 1ps

module full_adder
input A,B,Cin,
output S,Cout
);

assign S = (A ^ B) ^ Cin;
assign Cout = (B & Cin) | (A & B);

endmodule
```

register\_logic.v

```
`timescale 1ns / 1ps

module register_logic
input clk,
input enable,
input [4:0] Data,
output reg [4:0] Q
);

initial Q = 0;
wire [4:0] Qin;
assign Qin = enable ? Data : Q;

//Sequential logic
always @(posedge clk) begin
Q <- Qin;
end

endmodule
```

ii. TB

```
`timescale 1ns / 1ps

module TB_RCA_4bits;

reg clk;
reg enable;
reg [3:0] A,B;
reg Cin;
wire [4:0] Q;

RCA_4bits u1 (
.clk(clk),
.enable(enable),
.A(A),
.B(B),
.Cin(Cin),
.Q(Q)
);

initial
begin

clk = 0;
enable = 0;

//Test 1
#10
A = 4'b0001;
B = 4'b0111;
Cin = 0;

#10

enable = 1;

//Test 2
#10
A = 4'b0111;
B = 4'b0111;
Cin = 0;

//Test 3
#10
A = 4'b1000;
B = 4'b0111;
Cin = 1;

//Test 4
#10
A = 4'b1100;
B = 4'b0100;
Cin = 0;

//Test 5
#10
A = 4'b1000;
B = 4'b1100;
Cin = 1;

//Test 6
#10
A = 4'b1001;
B = 4'b1010;
Cin = 1;

//Test 7
#10
A = 4'b1111;
B = 4'b1111;
Cin = 0;

end

always
#5 clk = ~clk;

endmodule
```

iii.

A[3:0]	B[3:0]	Cin	Sum[3:0]	Cout
0001	0101	0	0110	0
0111	0111	0	1110	0
1000	0111	1	0000	1
1100	0100	0	0000	1
1000	1000	1	0001	1
1001	1010	1	0010	1
1111	1111	0	1110	1

iv.

```
set_property PACKAGE_PIN W5 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports clk]
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports clk]

set_property PACKAGE_PIN V17 [get_ports {A[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {A[0]}]
set_property PACKAGE_PIN V16 [get_ports {A[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {A[1]}]
set_property PACKAGE_PIN W16 [get_ports {A[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {A[2]}]
set_property PACKAGE_PIN W17 [get_ports {A[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {A[3]}]
set_property PACKAGE_PIN W15 [get_ports {B[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[0]}]
set_property PACKAGE_PIN V15 [get_ports {B[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[1]}]
set_property PACKAGE_PIN W14 [get_ports {B[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[2]}]
set_property PACKAGE_PIN V13 [get_ports {B[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {B[3]}]
set_property PACKAGE_PIN V2 [get_ports {Cin}]
set_property IOSTANDARD LVCMOS33 [get_ports {Cin}]

set_property PACKAGE_PIN U16 [get_ports {Q[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[0]}]
set_property PACKAGE_PIN E19 [get_ports {Q[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[1]}]
set_property PACKAGE_PIN V19 [get_ports {Q[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[2]}]
set_property PACKAGE_PIN V19 [get_ports {Q[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[3]}]
set_property PACKAGE_PIN W18 [get_ports {Q[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q[4]}]

set_property PACKAGE_PIN U18 [get_ports enable]
set_property IOSTANDARD LVCMOS33 [get_ports enable]
```

v.



Part 2

vi. Cost:

$C_1 = G_0 + P_0 C_0$

$C_2 = G_1 + G_0 P_1 + P_0 P_1 C_0$

$C_3 = G_2 + G_1 P_2 + G_0 P_1 P_2 + P_0 P_1 P_2 C_0$

$C_4 = G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + P_0 P_1 P_2 P_3 C_0$

Sum:

$S_0 = P_0 \hat{C}_0$

$S_1 = P_1 \hat{C}_1$

$S_2 = P_2 \hat{C}_2$

$S_3 = P_3 \hat{C}_3$

Work

$$S_0 = P_0 \hat{C}_0 = P_0 (G_0 + P_0 C_0) = P_0 G_0 + P_0^2 C_0$$
$$S_1 = P_1 \hat{C}_1 = P_1 (G_1 + G_0 P_1 + P_0 P_1 C_0) = P_1 G_1 + P_1 G_0 P_1 + P_0 P_1^2 C_0$$
$$S_2 = P_2 \hat{C}_2 = P_2 (G_2 + G_1 P_2 + G_0 P_1 P_2 + P_0 P_1 P_2 C_0) = P_2 G_2 + P_2 G_1 P_2 + P_2 G_0 P_1 P_2 + P_0 P_1 P_2^2 C_0$$
$$S_3 = P_3 \hat{C}_3 = P_3 (G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + P_0 P_1 P_2 P_3 C_0) = P_3 G_3 + P_3 G_2 P_3 + P_3 G_1 P_2 P_3 + P_3 G_0 P_1 P_2 P_3 + P_0 P_1 P_2 P_3^2 C_0$$

vii.

CLA\_4bits.v

register\_logic.v

Same as above

```
`timescale 1ns / 1ps

module CLA_4bits
input clk,
input enable,
input [3:0] A,B,
input Cin,
output [4:0] Q
);

wire [3:0] G, P;
wire [4:0] C;
wire [4:0] Sum;
wire Cout;

assign C[0] = Cin;

assign G[0] = A[0] & B[0];
assign G[1] = A[1] & B[1];
assign G[2] = A[2] & B[2];
assign G[3] = A[3] & B[3];

assign P[0] = A[0] ^ B[0];
assign P[1] = A[1] ^ B[1];
assign P[2] = A[2] ^ B[2];
assign P[3] = A[3] ^ B[3];

assign C[1] = G[0] | (P[0] & C[0]);
assign C[2] = G[1] | (G[0] & P[1]) | (P[0] & P[1] & C[0]);
assign C[3] = G[2] | (G[1] & P[2]) | (G[0] & P[1] & P[2]) | (P[0] & P[1] & P[2] & C[0]);
assign C[4] = G[3] | (G[2] & P[3]) | (G[1] & P[2] & P[3]) | (G[0] & P[1] & P[2] & P[3]) | (P[0] & P[1] & P[2] & P[3] & C[0]);

assign Sum[0] = P[0] ^ C[0];
assign Sum[1] = P[1] ^ C[1];
assign Sum[2] = P[2] ^ C[2];
assign Sum[3] = P[3] ^ C[3];
assign Sum[4] = C[4];

register_logic r0(clk,enable(enable),Data(Sum),Q[Q]);

endmodule
```

viii.

TB

```
`timescale 1ns / 1ps

module TB_CLA_4bits;

reg clk;
reg enable;
reg [3:0] A,B;
reg Cin;
wire [4:0] Q;

CLA_4bits u1 (
.clk(clk),
.enable(enable),
.A(A),
.B(B),
.Cin(Cin),
.Q(Q)
);

initial
begin

clk = 0;
enable = 0;

//Test 1
#10
A = 4'b0101;
B = 4'b0111;
Cin = 0;

#10

enable = 1;

//Test 2
#10
A = 4'b1001;
B = 4'b0100;
Cin = 1;

//Test 3
#10
A = 4'b1001;
B = 4'b1001;
Cin = 0;

//Test 4
#10
A = 4'b1001;
B = 4'b0100;
Cin = 0;

//Test 5
#10
A = 4'b1000;
B = 4'b1000;
Cin = 1;

//Test 6
#10
A = 4'b1101;
B = 4'b1010;
Cin = 1;

//Test 7
#10
A = 4'b1111;
B = 4'b1111;
Cin = 0;

end

always
#5 clk = ~clk;


endmodule
```

ix.

A[3:0]	B[3:0]	Cin	Sum[3:0]	Cout
0000	0101	0	0101	0
1000	0111	1	0000	1
1001	0100	0	1101	0
1000	1000	1	0001	1
1001	1010	1	0100	1
1111	1111	0	1110	1


x. Constraints same as above

xi.

 


Part 3

xii. Part 1

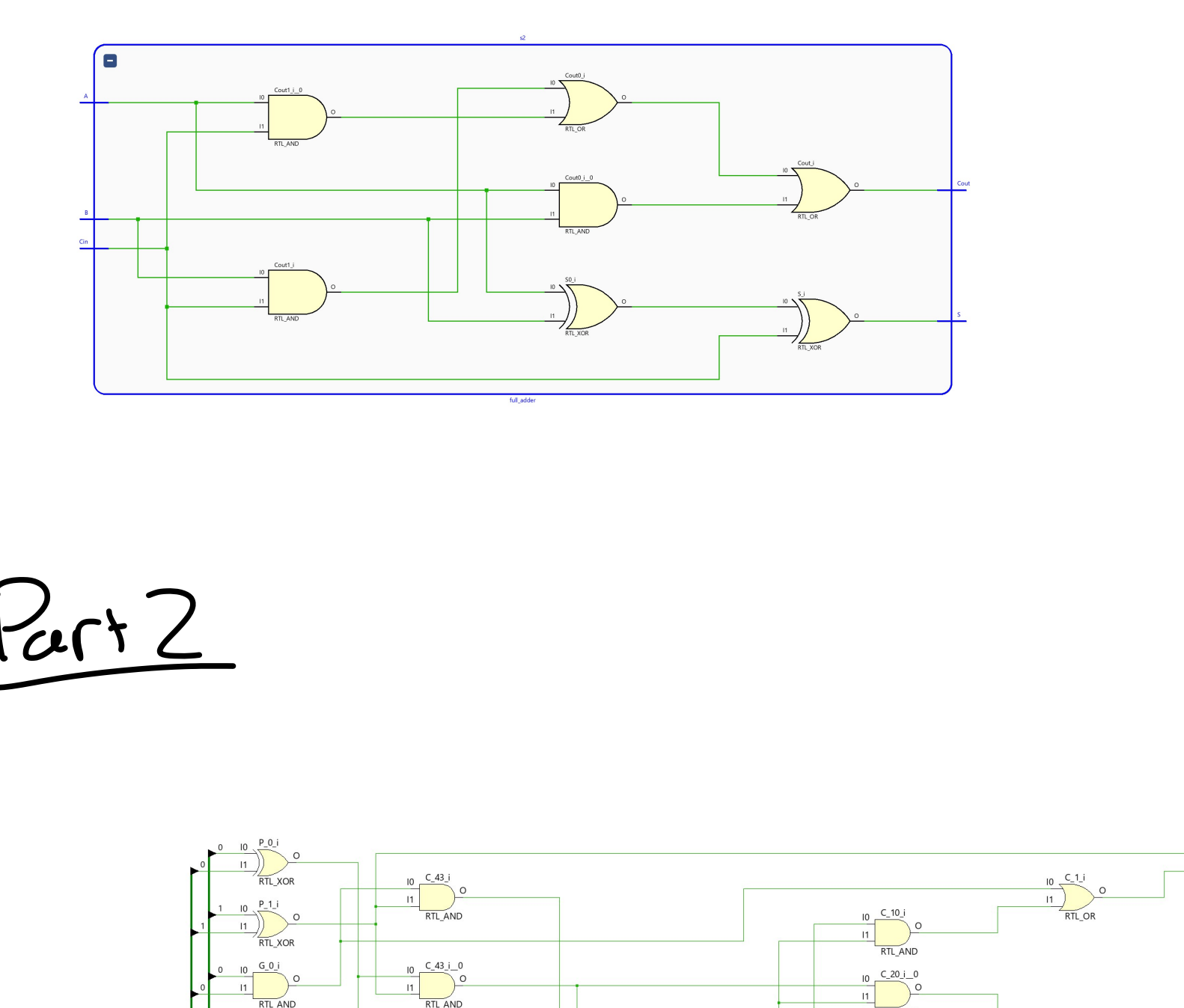

Part 2

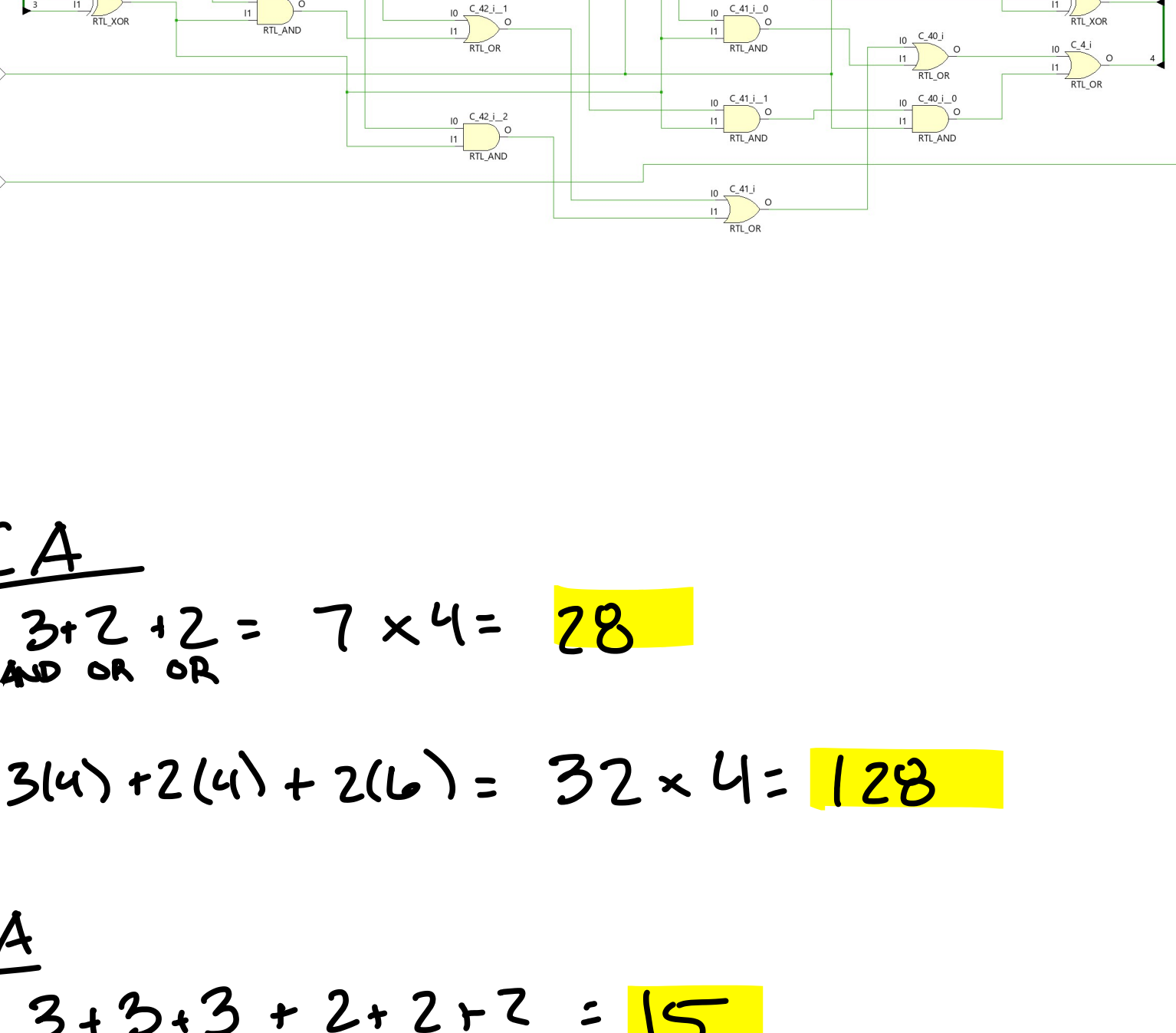

xiii.

RCA

Delay:  $3\tau + 2\tau = 7 \times 4 = 28$

Area:  $3(4) + 2(4) + 2(6) = 32 \times 4 = 128$

CLA

Delay:  $3 + 3 + 3 + 2 + 2 + 2 = 15$

Area:  $8(6) + 17(4) + 10(4) = 156$

xiv. CLA is faster because don't have to wait for the Cout to ripple through. However to do this involves more gates so our area increases for CLA

RCA: good for constrained space, better readability, performance not critical

CLA: performance is most important